


# Simple Circuits

Name: \_\_\_\_\_

Date: \_\_\_\_\_

Aim: To find out how a simple circuit can be connected.

Equipment I used:

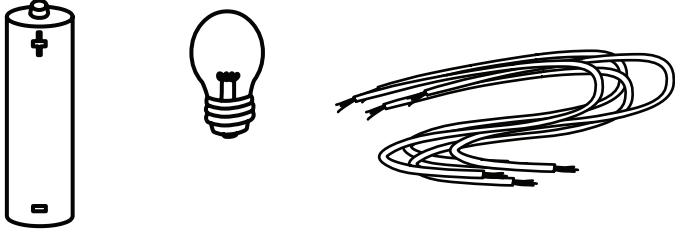

Draw:

What I did:

What happened:

I discovered that...

